



Click to view this week's ad screen

[Ideas For Design]

Optically Isolated 4- To 20-mA Current-Loop Transmitter Is Accurate, Inexpensive

W. Stephen Woodward

ED Online ID #19676

September 25, 2008

Copyright © 2006 Penton Media, Inc., All rights reserved.

Printing of this document is for personal use only.



Galvanically (that is, optically or electromagnetically) isolated 4- to 20-mA current loops offer robust noise immunity and tolerate long cable runs. These advantages, combined with simple unshielded two-wire cabling, make this mature signaling standard popular for transmitting analog data in noisy industrial and process control environments. Unfortunately, the conversion of an analog voltage output to an isolated current-loop signal is relatively complicated. In addition to the actual signal isolator components, multiple floating power supplies are typically required.

The current-loop transmitter in the figure employs an unusual trick to inexpensively implement an optically isolated 4- to 20-mA transmitter: operation of the quad-channel LED/transistor optoisolator (an NEC PS2501-4) in a linear mode. Normally, this would be a dubious idea because LED/transistor optoisolator response is typically very nonlinear and temperature-dependent, making it incompatible with accurate transmission of precision analog data.

Working around this limitation and achieving adequate analog accuracy from this class of component requires meeting two goals:

- Nonlinearity and temperature-coefficient compensation through feedback matching of reference elements in a multichannel microcircuit so that nonlinearities will cancel.
- Scrupulous duplication and tracking of operating points (voltage and current bias) of the reference elements.

The first is achieved by matching LED/transistor pair U2c to U2a, b, and d. U2c is part of the feedback loop of op-amp U1, causing the LED drive current to be controlled so that $I_3 = I_{IN}$. Because all four LEDs in U2 are serially connected, the other three optical pairs receive an identical LED drive current, causing their phototransistors to conduct the same collector currents. That is:

$$I_1 = I_2 = I_3 = I_4 = I_{IN}, \text{ which is 0 to 5.33 mA}$$

However, this equality depends not only on the physical matching of the four U2 channels, but also on the match of their bias voltages, which is the second design goal. This goal is achieved through the equality of the 1.25-V set point of U1 to the 1.25-V internal reference of regulator U4.

Remaining circuit details include calibration trims for

The industry leader
in Flash technology.

Photos | Music | Video | Data



> What can you
do with flash?

SAMSUNG

minimum (4 mA) and full-scale (20 mA) output currents and the option of operation with an external loop-voltage supply (passive mode) or with the dc-dc converter, U3 (active mode). I_{SUM} is:

$$3(I_{IN} + I_{MIN}) = (0 \text{ to } 16 \text{ mA}) + 4 \text{ mA} = 4 \text{ to } 20 \text{ mA}$$


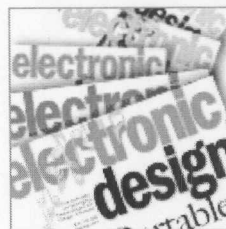


fig 1

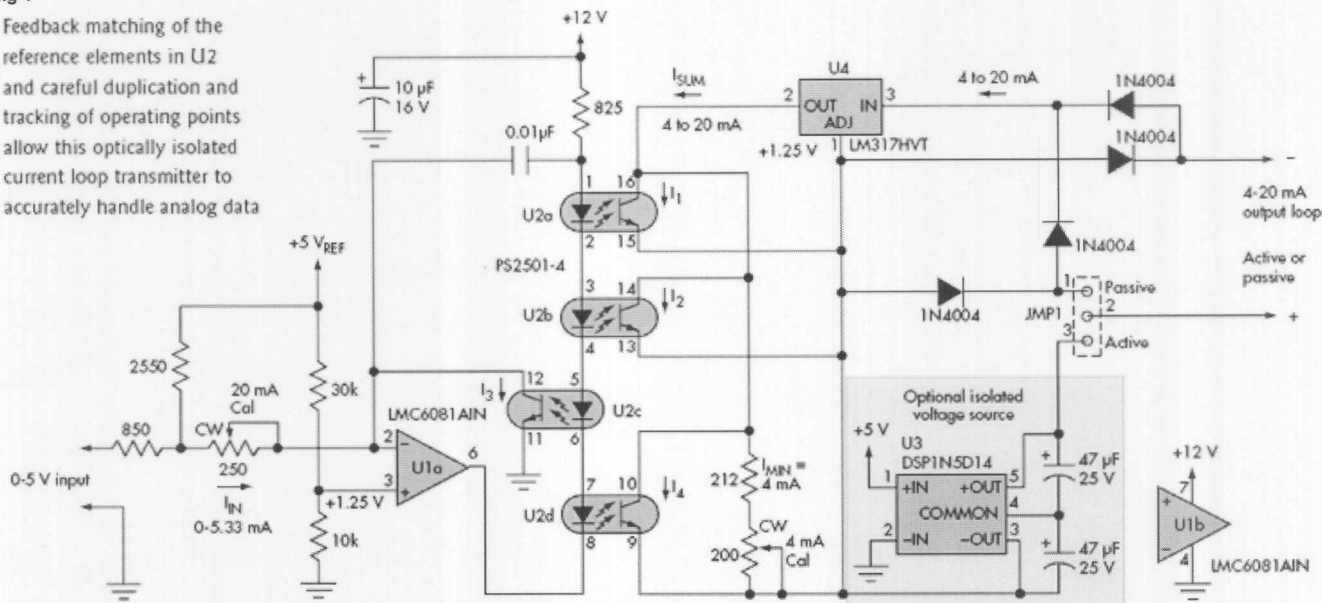Feedback matching of the reference elements in U2 and careful duplication and tracking of operating points allow this optically isolated current loop transmitter to accurately handle analog data



PartFinder



Find real-time pricing, stock status, same-day/next-day shipping options and more. Brought to you by **Digi-Key**. [Go to PartFinder](#). Enter Search Term Here

GlobalSpec

PART SEARCH :

Powered by: **GLOBALSPEC**

Tackle the Challenges of RFID Testing with help from Tektronix

New from Tektronix: Solving the Most Difficult RFID Testing Challenges app note. It offers a systematic and detailed approach to resolving the toughest RFID challenges using Tektronix Real-Time Spectrum Analyzers. Request your copy today!

Free Measurement and Control Handbook

Keithley's "Understanding New Developments in Measurement, and Control," is a guide to high-performance test and measurement applications and techniques. Order your copy by calling 1-800-588-9238.

Download Free Whitepapers and eBooks

Check out the full selection of whitepapers and ebooks available today on Electronic Design

Sponsored Links

Electronic Circuit Design
Transform your idea to reality! We design
Electronics 877-923-9009
www.astinco.com


Electronic Design
IENSO is a provider of electronic design and
manufacturing services
www.iensco.com

Circuit Design
Register Now & Get the Job You Want Dice -
Career Hub for Tech Insiders
www.Dice.com

Custom Electronic Designs
Control Electronics and Programming Design
to Prototype Quickly
www.gunnsys.com

Component Datasheets
Product Models and Purchasing Info. Browse
Data from Over 1000 Sources!
SupplyFrame.com

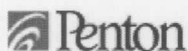Electronic Design Europe Electronic Design China EEPN Power Electronics Auto Electronics Microwaves & RF
Mobile Dev & Design Schematics Find Power Products Military Electronics EE Events Related Resources



[Planet EE Network](#) | [Contact Us](#) | [Editorial Calendar](#) | [Media Kit](#) | [Submit Articles](#) | [Headlines](#) | [Site Feedback](#) | [Subscribe](#)
[Advanced Search](#) | [Help](#) | [Site Map](#)

Copyright © 2008 Penton Media, Inc., All rights reserved. [Privacy](#)